

Filtro	Función de aproximación	Retardo constante	Desvío del retardo máximo	Atenuación máxima
E	Bessel	80 μ s	5% @ 3 kHz	1 dB @ 2 kHz

• Con un filtro $n=3$ deberíamos llegar.

$$\begin{aligned}
 \cdot \cotgh(s) &= \frac{\cosh(s)}{\sinh(s)} = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{s}{5}} \\
 &= \frac{1}{s} + \frac{s5}{15 + s^2} \\
 &= \frac{s^2 + 15 + s^25}{s^3 + s15} \\
 &= \frac{s^26 + 15}{s^3 + s15}
 \end{aligned}$$

$$\cdot T(s) = \frac{1}{\cosh(s) + \sinh(s)} = \frac{15}{s^3 + s^26 + s15 + 15}$$

$$T(s) \Big|_{s=j\omega} = \frac{15}{-j\omega^3 - \omega^26 + j\omega15 + 15} = \frac{15}{(15 - \omega^26) + j(\omega15 - \omega^3)}$$

$$|T(j)| = \frac{15}{\sqrt{9^2 + 14^2}} = \frac{15}{\sqrt{277}} = 0,9012$$

$$\cdot \alpha_{\max}(j) = -20 \cdot \log(|T(j)|) = 0,903 \text{ dB}$$

$$\cdot \phi(\omega) = -\tan^{-1}\left(\frac{\omega15 - \omega^3}{15 - \omega^26}\right)$$


$$\cdot D(\omega) = \frac{-d\phi(\omega)}{d\omega} = \frac{225 + 45\omega^2 + 6\omega^4}{225 + 45\omega^2 + 6\omega^4 + \omega^6}$$

$$\cdot \text{Error}(\%) = \left| \frac{D(\omega_s) - D(0)}{D(0)} \right| = \left| \frac{0,968 - 1}{1} \right| = 3,2\%$$

$$\therefore T(s) = \frac{6,45944 \cdot 2,32219}{(s^2 + 3,67782 + 6,45944)(s + 2,32219)}$$

$\hookrightarrow Q = 0,691$

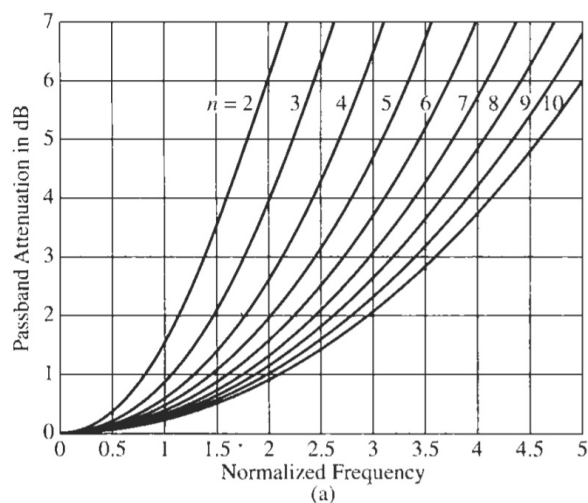
• se propone el siguiente circuito (en función del Q)



$$\cdot \omega_0 = \frac{1}{\tau_0} = \frac{1}{80\mu s} = 12500 \text{ rad/s}$$

$$\cdot \omega_c = \frac{2\pi \cdot 2 \text{ kHz}}{12500 \text{ r/s}} = 1 \text{ r/s}$$
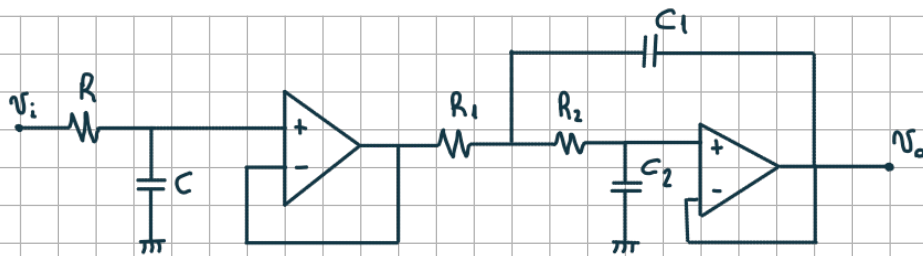
$$\cdot \omega_s = \frac{2\pi \cdot 3 \text{ kHz}}{12500 \text{ r/s}} = 1,507 \text{ r/s}$$



• RC

$$\cdot T(s) = \frac{1/sC}{\frac{1}{sC} + R} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$\cdot \Omega_\omega = \omega_0 \quad \therefore \frac{1}{RC} = 1$$

• con $C = 1$, $R = 1$

• Sallen Key

$$\cdot T(s) = \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \frac{1}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\cdot \Omega_\omega = \omega_0$$

$$\cdot 1 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\cdot \text{con } C_2 = 1, \quad R_1 = \frac{1}{R_2 C_1}$$

$$\cdot \frac{1}{Q} = \frac{1}{C_1} \left(R_2 C_1 + \frac{1}{R_2} \right)$$

$$\frac{1}{Q} = R_2 + \frac{1}{R_2 C_1}$$

$$0 = R_2^2 - \frac{R_2}{Q} + \frac{1}{C_1}$$

• Corroboro que valor de C_1 da raíces positivas

$$\frac{R_2^2}{Q^2} - 4 \cdot R_2^2 \cdot \frac{1}{C_1} > 0$$

$$R_2^2 \left(\frac{1}{Q^2} - \frac{4}{C_1} \right) > 0$$

$$\frac{1}{Q^2} > \frac{4}{C_1}$$

$$C_1 > 4Q^2$$

$$C_1 > 1,909$$

Propongo $C_1 = 2,2$ (sabiendo valores comerciales)


• Retorno: $\frac{1}{Q} = R_2 + \frac{1}{R_2 C_1}$

$\therefore R_2 = 0,4608$

• Retorno: $R_1 = \frac{1}{R_2 C_1}$

$R_1 = 0,9864$

• EL circuito queda:

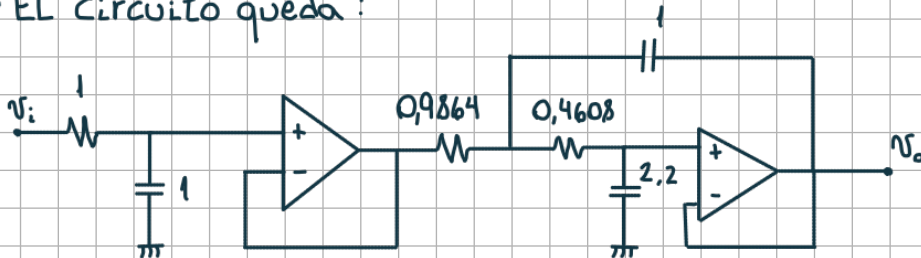

• Desnormalización ($\Omega_w = 12500 \text{ }^\circ/\text{s}$)

• RC

• H: $\Omega_w = 12500 \text{ }^\circ/\text{s} \cdot 2,32219 = 29027 \text{ }^\circ/\text{s}$

• Quiero un $C = 1 \text{ nF}$

• $C_r = \frac{C_n}{\Omega_w \cdot \Omega_z} \rightarrow 1 \text{ nF} = \frac{1}{29027 \text{ }^\circ/\text{s} \cdot \Omega_z}$

$\Omega_z = 34,45 \text{ K}\Omega$

• $R_r = R_n \cdot \Omega_z = 34,45 \text{ K}\Omega$

$\hookrightarrow$ Valor comercial = 33 K

• Sallen Key


• $\Omega_w = 12500 \text{ }^\circ/\text{s} \cdot \sqrt{6,45944} = 31769 \text{ }^\circ/\text{s}$

• Quiero un $C_{2r} = 1 \text{ nF}$, $\therefore \Omega_z = 31477 \Omega$

• $R_{1r} = 31 \text{ K}\Omega \rightarrow V_C = 33 \text{ K}\Omega$

• $R_{2r} = 14,5 \text{ K}\Omega \rightarrow V_C = 15 \text{ K}\Omega$

• Finalmente

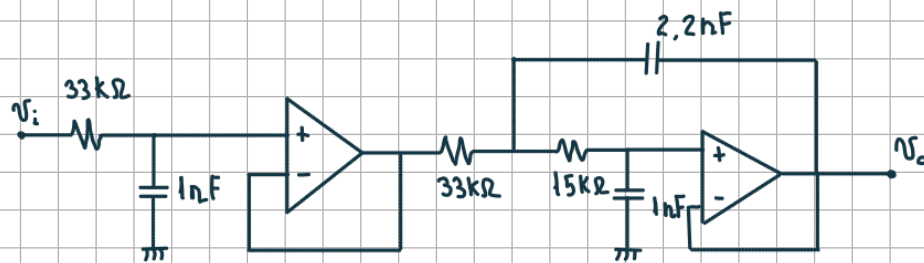

• LTSpice

